

### Transistor Hybrid Model for AC Analysis

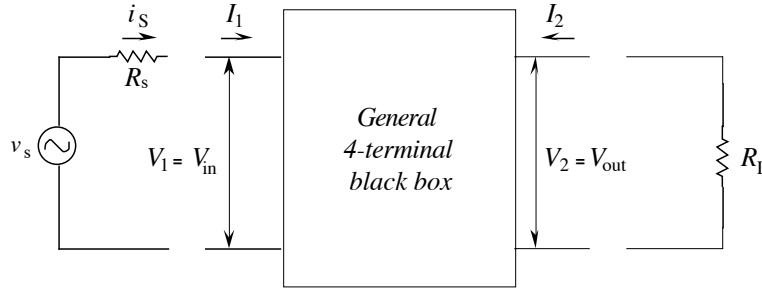


Figure 1

There are four variables:  $I_1$ ,  $V_1$ ,  $I_2$ , and  $V_2$ ; they represent the instantaneous values of the currents and voltages. We can write two Kirchhoff voltage equations.

One for the input loop 
$$f(I_1, V_1, I_2, V_2) = 0$$

and

one for the output loop 
$$g(I_1, V_1, I_2, V_2) = 0.$$

The exact form of the function  $f$  and  $g$  will depend on the contents of the black box. We will pick two of the four variables to be independent ( $I_1$ ,  $V_2$ ) and two to be dependent ( $I_2$ ,  $V_1$ ). Starting with the function  $f$  we solve for  $V_1$ , then substitute  $V_1$  into function  $g$ . Finally, we solve for  $I_2$  in terms of  $I_1$ , and  $V_2$ . In a similar manner we can eliminate  $I_2$  and solve for  $V_1$  in terms of  $I_1$ , and  $V_2$ . We obtain the following general functions

$$I_2 = I_2(I_1, V_2) \quad \text{and} \quad V_1 = V_1(I_1, V_2).$$

In general we are interested in the response of the transistor to the application of small, low frequency AC input signals (differential changes). To obtain the expressions for the change in  $I_2$  and  $V_1$  as a function of the changes in  $I_1$  and  $V_2$  we take the differentials of the above functions.

*Model Equations:*  $V_1 = V_1(I_1, V_2)$  and  $I_2 = I_2(I_1, V_2)$

$$dI_2 = \left( \frac{\partial I_2}{\partial I_1} \right)_{V_2} dI_1 + \left( \frac{\partial I_2}{\partial V_2} \right)_{I_1} dV_2 \quad \text{and} \quad dV_1 = \left( \frac{\partial V_1}{\partial I_1} \right)_{V_2} dI_1 + \left( \frac{\partial V_1}{\partial V_2} \right)_{I_1} dV_2$$

Letting lower case letters represent small AC voltages and currents

$$i_1 \equiv dI_1 \quad i_2 \equiv dI_2 \quad v_1 \equiv dV_1 \quad \text{and} \quad v_2 \equiv dV_2$$

and defining hybrid parameters  $h_{xy}$  yields

$$i_2 = \left( \frac{\partial I_2}{\partial I_1} \right)_{V_2} i_1 + \left( \frac{\partial I_2}{\partial V_2} \right)_{I_1} v_2 = h_{21} i_1 + h_{22} v_2$$

and

$$v_1 = \left( \frac{\partial V_1}{\partial I_1} \right)_{V_2} i_1 + \left( \frac{\partial V_1}{\partial V_2} \right)_{I_1} v_2 = h_{11} i_1 + h_{12} v_2.$$

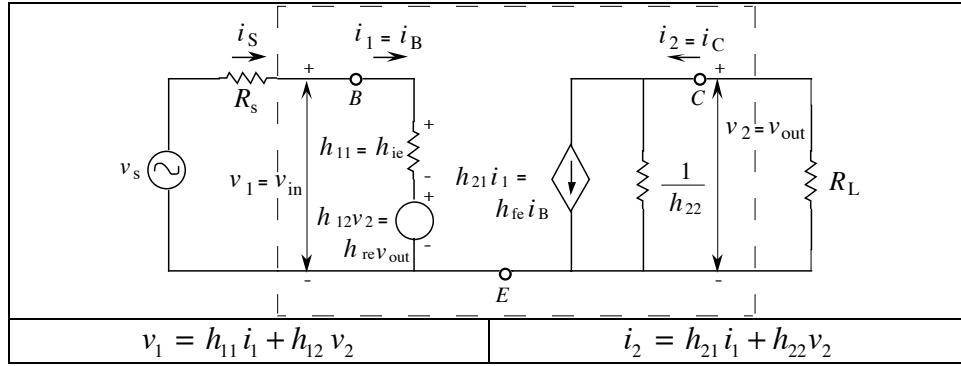


Figure 2

$h_{21} \equiv \left( \frac{\partial I_2}{\partial I_1} \right)_{V_2}$	a pure number <i>forward current transfer ratio</i>	represents how much of the input current $i_1$ is transferred to the output current $i_2$ ; The higher the value of $h_{21}$ , the larger the change in output current for a given input current change.
$h_{22} \equiv \left( \frac{\partial I_2}{\partial V_2} \right)_{I_1}$	a conductance <i>output admittance</i>	an admittance or conductance directly across the output terminals
$h_{11} \equiv \left( \frac{\partial V_1}{\partial I_1} \right)_{V_2}$	a resistance <i>input resistance</i>	a resistance in the input circuit; it is usually called the input resistance
$h_{12} \equiv \left( \frac{\partial V_1}{\partial V_2} \right)_{I_1}$	a pure number <i>reverse voltage transfer ratio</i>	the amplitude of a voltage generator in the input; it represents how much of the output voltage $v_2$ is fed back into the input

Table 1

This mathematical development is exact; that is, no approximations have been made except that  $v$  and  $i$  must refer to small signals because the starting equations hold exactly only for infinitesimal changes in  $v$ 's and  $i$ 's. To show that this mathematical model can represent a *real* transistor a comparison of experimental *input* and *output* curves for a transistor must be looked at and  $h_{xy}$  values based on these curves must be chosen. The model will represent the real transistor if for a chosen set of  $h_{xy}$  parameters they represent the experimental curves over a wide range of currents and voltages.

The mathematical model developed above is a four terminal device while a transistor is a three terminal device. To apply this model to a transistor two of the terminals must be

common between the input and output. Three configurations are possible: common emitter, common collector, and common base. The  $h_{xy}$  parameters will be different for each configuration. When a configuration is chosen letter subscripts are usually used instead of the numerical subscripts. The second letter denotes which terminal is common. In general the values of a particular  $h_{xy}$  are different for each configuration, e.g.,  $h_{fe} \neq h_{fb}$ .


<b><i>h</i> Parameter Notation</b>			
<b><i>h</i> parameter</b>	<b>CE</b>	<b>CC</b>	<b>CB</b>
$h_{11}$	$h_{ie}$	$h_{ic}$	$h_{ib}$
$h_{12}$	$h_{re}$	$h_{re}$	$h_{rb}$
$h_{21}$	$h_{fe}$	$h_{fc}$	$h_{fb}$
$h_{22}$	$h_{oe}$	$h_{oc}$	$h_{ob}$
	<i>Common Emitter</i>	<i>Common Collector</i>	<i>Common Base</i>

Table 2

<b>Equations for transistor alone</b> (no biasing, collector, emitter, or load resistors)	
<i>Voltage Gain</i>	$A_v = \frac{-h_{21}R_L}{(h_{11}h_{22} - h_{12}h_{21})R_L + h_{11}}$
<i>Current Gain</i>	$A_i = \frac{h_{21}}{1 + h_{22}R_L}$
<i>Input Impedance</i>	$Z_{T_{in}} = \frac{(h_{11}h_{22} - h_{12}h_{21})R_L + h_{11}}{1 + h_{22}R_L}$
<i>Output Impedance</i>	$Z_{T_{out}} = \frac{h_{11} + R_S}{(h_{11}h_{22} - h_{12}h_{21}) + h_{22}R_S}$

<b>Approximate Gains &amp; Impedances for Transistor Circuits</b>			
	<b>CE</b>	<b>CC</b>	<b>CB</b>
$A_v$	$-\frac{h_{fe}(R_C \parallel R_L)}{h_{ie}} \approx -h_{fe} \approx 100$	1	$\frac{h_{fe}R_L}{h_{ie}} \approx h_{fe} \approx 100$
$A_i$	$h_{fe} \approx 100$	$-h_{fe} \approx -100$	1
$Z_{in}$	$h_{ie} \parallel R_1 \parallel R_2$	$\sim h_{fe}(R_E \parallel R_L \parallel R_1 \parallel R_2)$	$\frac{h_{ie}}{h_{fe}} \parallel R_1 \parallel R_2$
$Z_{out}$	$\frac{h_{ie}}{(h_{11}h_{22} - h_{12}h_{21})} \parallel R_C \cong 5k\Omega \parallel R_C$	$\sim \frac{h_{ie}}{h_{fe}} \parallel R_E$	$\frac{h_{fe}R_S}{h_{11}h_{22} - h_{12}h_{21}} \parallel R_C$

## Common Emitter Configuration

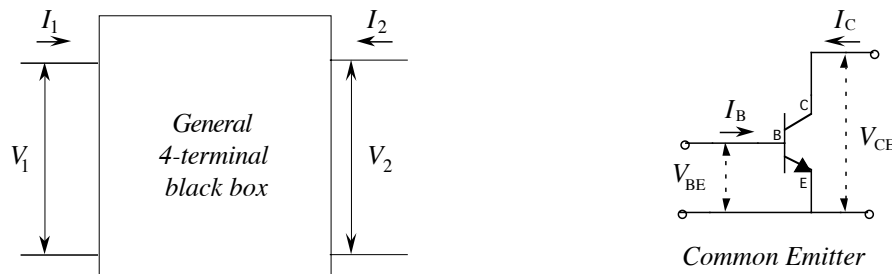

$$I_1 \rightarrow I_B, \quad V_1 \rightarrow V_{BE}, \quad I_2 \rightarrow I_C, \quad V_2 \rightarrow V_{CE}$$

Figure 3

The experimental curves we look at are  $I_C = I_C(I_B, V_{CE})$  and  $V_{BE} = (I_B, V_{CE})$ .

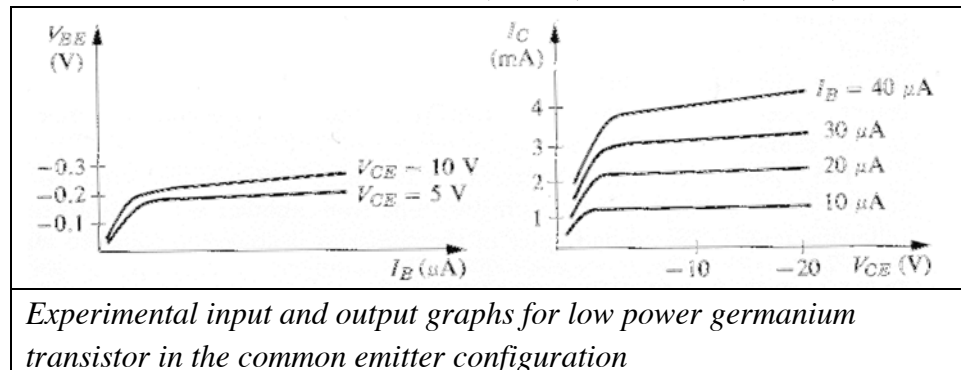


Figure 4

<b>Common Emitter Configuration</b>		
$h_{21} \equiv \left( \frac{\partial I_2}{\partial I_1} \right)_{V_2} \Rightarrow h_{fe} = \left( \frac{\partial I_C}{\partial I_B} \right)_{V_{CE}}$	<i>forward current transfer ratio</i> (a pure number)	$h_{fe} \approx 100$ AC current gain $h_{FE} = \beta = \frac{I_C}{I_B}$ DC current gain $h_{fe} \approx h_{FE}$ roughly constant for $ V_{CE}  \geq 1V$ although; it increases slightly as $I_C$ increases. It decreases drastically when $ V_{CE} $ is well below 1V. Choose a quiescent point with $V_{CE}$ greater than 1V.
$h_{22} \equiv \left( \frac{\partial I_2}{\partial V_2} \right)_{I_1} \Rightarrow h_{oe} = \left( \frac{\partial I_C}{\partial V_{CE}} \right)_{I_B}$	<i>output admittance</i> (a conductance)	$h_{oe} \approx 2 \times 10^{-5}$ siemens For $V_{CE} > 1V$ it is essentially constant. It does increase with an increase in $I_C$
$h_{11} \equiv \left( \frac{\partial V_1}{\partial I_1} \right)_{V_2} \Rightarrow h_{ie} = \left( \frac{\partial V_{BE}}{\partial I_B} \right)_{V_{CE}}$ $= \left( \frac{\partial I_B}{\partial V_{BE}} \right)_{V_{CE}}^{-1}$ $h_{11} = \left( \frac{\partial V_1}{\partial I_1} \right)_{V_2} = \left( \frac{\partial V_1}{\partial I_2} \frac{\partial I_2}{\partial I_1} \right)_{V_2} = h_{21} \left( \frac{\partial V_1}{\partial I_2} \right)_{V_2}$ $\frac{h_{11}}{h_{21}} = \left( \frac{\partial V_1}{\partial I_2} \right)_{V_2} \Rightarrow \frac{h_{ie}}{h_{fe}} = \left( \frac{\partial V_{BE}}{\partial I_C} \right)_{V_{CE}}$	<i>input resistance</i> (a resistance)	$h_{ie} = \frac{kT}{eI_B} = \frac{\beta kT}{eI_C}$ $h_{ie} (\beta = 100, T = 300^\circ K) = \frac{2.59}{I_C}$ $v_{BE} = i_B h_{ie}$ where $h_{ie}$ is the effective AC resistance of the forward biased base-emitter diode junction. $h_{ie}$ is typically $2.6k\Omega$ for $I_C = 1$ mA, and $h_{ie}$ varies inversely with $I_C$ ( $h_{ie} = 260\Omega$ for $I_C = 10$ mA).
$h_{12} \equiv \left( \frac{\partial V_1}{\partial V_2} \right)_{I_1} \Rightarrow h_{re} = \left( \frac{\partial V_{BE}}{\partial V_{CE}} \right)_{I_B}$	<i>reverse voltage transfer ratio</i> (a pure number)	$h_{re} \approx 10^{-4}$ represents how much of the output voltage $v_2$ is fed back into the input; roughly constant for $I_B > 10\mu A$

Table 3

The  $h_{xy}$  parameters are essentially constant when  $V_{CE} > 1V$ ,  $I_B > 10\mu A$  ( $I_C > 1$  mA).

Application of Kirchhoff's and Ohm's Laws	
(a) $v_1 = h_{11} i_1 + h_{12} v_2$	(c) $i_2 = h_{21} i_1 + h_{22} v_2$
(b) $v_s = (R_s + h_{11}) i_1 + h_{12} v_2$	(d) $v_2 = -i_2 (R_C \parallel R_L)$

Table 4

### Voltage Gain

The voltage gain is defined as  $A_v \equiv v_{out}/v_{in} = v_2/v_1$ . Using equations (a) – (d) we obtain

$$i_2 = -\frac{v_2}{(R_C \parallel R_L)} = h_{21} i_1 + h_{22} v_2 \quad \text{and} \quad i_1 = \frac{v_1 - h_{12} v_2}{h_{11}} = \frac{v_s - h_{12} v_2}{(R_s + h_{11})}$$

Substituting for  $i_1$

$$-\frac{v_2}{(R_C \parallel R_L)} = h_{21} \left( \frac{v_1 - h_{12} v_2}{h_{11}} \right) + h_{22} v_2$$

and solving for  $v_2/v_1$

$$A_v = \frac{v_2}{v_1} = \frac{h_{21}}{h_{12} h_{21} - h_{11} h_{22} - \frac{h_{11}}{R_C \parallel R_L}} = \frac{h_{fe}}{h_{re} h_{fe} - h_{ie} h_{oe} - \frac{h_{ie}}{R_C \parallel R_L}}$$

For typical values for a low power transistor

$$A_v \approx \frac{-h_{21}}{h_{11}} R_C \parallel R_L = \frac{-h_{fe}}{h_{ie}} R_C \parallel R_L$$

### Current Gain

The current gain is defined as  $A_i \equiv i_2/i_1$ . substituting  $-i_2 (R_C \parallel R_L)$  for  $v_2$  yields

$$i_2 = h_{21} i_1 + [-i_2 (R_C \parallel R_L)] h_{22}$$

Solving for  $i_2/i_1$

$$A_i = \frac{i_2}{i_1} = \frac{h_{21}}{1 + h_{22} (R_C \parallel R_L)} = \frac{h_{fe}}{1 + h_{oe} (R_C \parallel R_L)}$$

### Input Impedance

Looking into the transistor

$$Z_{T_{in}} \equiv \frac{v_1}{i_1} = h_{11} - \frac{h_{12}h_{21}}{h_{22} + \frac{1}{R_C \parallel R_L}} \approx h_{11} = h_{ie} \text{ (for typical low power transistor values)}$$

values)

What the source  $v_s$  sees

The source drives both the transistor and the bias network. The impedance the source sees is

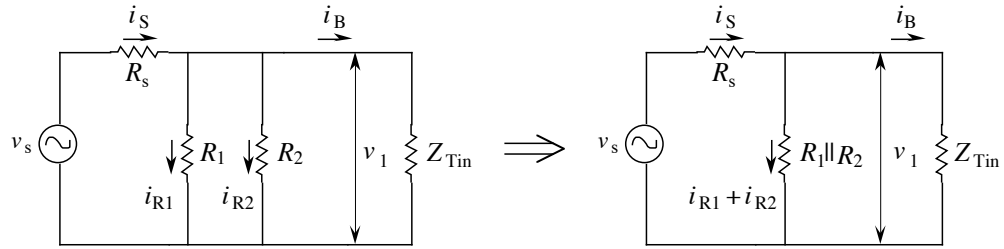


Figure 5

$$\frac{1}{Z_S} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{Z_{T_{in}}} \Rightarrow Z_{S_{in}} \approx Z_{T_{in}} \quad \text{if} \quad R_1 \parallel R_2 \gg Z_{T_{in}}$$

If  $R_1 \parallel R_2$  is small compared to  $Z_{T_{in}}$  then most of the current supplied by the signal source will flow through  $R_1 \parallel R_2$ , thus lowering the  $i_B$ . This results in lowering the transistor output (i.e, lowering the transistor gain).

### Output Impedance

The output impedance looking back into the two output terminals is important for two reasons:

1. Determines the high frequency response of the circuit (particularly when driving a capacitive load where it represents the resistance in a low-pass filter)
2. Determines how much power is transferred to the load attached to the two output terminals.

Another thing to note is that for a given fixed voltage source and a fixed transistor output impedance:

1. The output voltage across the load is maximum if  $R_L \gg Z_{T_{out}}$
2. The output current through the load will be a maximum when  $R_L \ll Z_{T_{out}}$
3. For purely a resistive load and output impedance of the transistor the output power through the load will be maximum when  $R_L = R_{out}$ . If the load is fixed, maximum power is delivered to the load when  $Z_{T_{out}} = 0$ .

To calculate the transistor output impedance in terms of the  $h_{xy}$  parameters we again start with the equations in Table 4.

$$v_s - i_1 R_s = v_1 = h_{11} i_1 + h_{12} v_2$$

$$i_2 = h_{21} i_1 + h_{22} v_2$$

If we let  $v_s$  be set to zero to avoid letting the output depend on the applied input signal ( $v_s=0$ ) then the transistor output impedance  $Z_{T_{out}} = v_2/i_2$  can be obtained by eliminating  $i_1$ .

$$-i_1 R_s = v_1 = h_{11} i_1 + h_{12} v_2$$

$$i_1 = -\frac{h_{12} v_2}{h_{11} + R_s}$$

$$i_2 = h_{21} i_1 + h_{22} v_2$$

$$i_2 = h_{21} \left( -\frac{h_{12} v_2}{h_{11} + R_s} \right) + h_{22} v_2$$

$$i_2 = \left\{ \frac{(h_{11} + R_s) h_{22} - h_{12} h_{21}}{h_{11} + R_s} \right\} v_2$$

$$Z_{T_{out}} \equiv \frac{v_2}{i_2} = \frac{h_{11} + R_s}{(h_{11} h_{22} - h_{12} h_{21}) + h_{22} R_s} = \frac{h_{ie} + R_s}{(h_{ie} h_{oe} - h_{re} h_{fe}) + h_{oe} R_s}$$

*Note:*

1. If the reverse voltage generator is not present ( $h_{12} = h_{re} = 0$ ) then  $Z_{T_{out}} = 1/h_{22} = 1/h_{oe}$  which is reasonable since  $h_{22}$  ( $h_{oe}$ ) is an admittance.
2. When  $h_{12} = h_{re} \neq 0$  then the transistor output impedance is a function of  $h_{11}$  ( $h_{ie}$ ) and  $R_s$  due to the coupling provided by  $h_{12}$  ( $h_{re}$ ).

The output impedance of a common emitter amplifier is  $Z_{out} = Z_{T_{out}} \parallel R_C \approx R_C$  when  $R_C$  is in the range of 2 to 20k $\Omega$

<b>P-N Junction</b>	
The current-voltage equation for a $p-n$ junction can be modeled as	
$I(V_B, T) = I_0 (e^{eV_B/kT} - 1)$	$e$ electronic charge, $1.60 \times 10^{-19}$ C $k$ Boltzmann's constant, $1.38 \times 10^{-23}$ J/ $^\circ$ K $T$ absolute temperature $^\circ$ K $V_B$ is positive for forward bias, negative for reverse bias $I_0$ the reverse current for large junction reverse bias
$I(V_B, T = 300^\circ K) = I_0 (e^{V_B/(25.875 mV)} - 1)$	$\left( \frac{kT}{e} \right)_{T=300^\circ K} = \frac{300 \times 1.38 \times 10^{-23}}{1.6 \times 10^{-19}} = 0.025875V$

Table 5



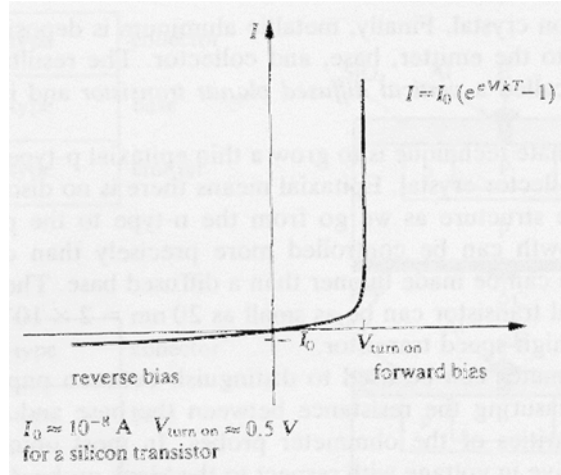


Figure 6

For the *base-emitter p-n junction* of the transistor the base-emitter current is

$$I_E(V_{BE}, T) = I_0 (e^{eV_{BE}/kT} - 1)$$

$$I_E(V_{BE}, T) = (\beta + 1) I_B$$

$$I_B(V_{BE}, T, \beta) = \frac{I_0}{(\beta + 1)} (e^{eV_{BE}/kT} - 1)$$

$$\frac{\partial I_B}{\partial V_{BE}} = \frac{e I_0}{(\beta + 1) kT} e^{eV_{BE}/kT}$$

$$V_{BE} = \frac{kT}{e} \ln \left( \frac{(\beta + 1) I_B}{I_0} + 1 \right)$$

$$h_{11} = \left( \frac{\partial V_1}{\partial I_1} \right)_{V_2} \Rightarrow h_{ie} = \left( \frac{\partial V_{BE}}{\partial I_B} \right)_{V_{CE}} = \left( \frac{\partial I_B}{\partial V_{BE}} \right)_{V_{CE}}^{-1} = \frac{(\beta + 1) kT}{e I_0} e^{-eV_{BE}/kT}$$



If  $V_{BE} > 0.6V$  or equivalently if  $I_B > 0.1\mu A$  then  $I_C > 10\mu A$ . The transistor is turned on and  $e^{eV_{BE}/kT} \gg 1$ . We can neglect the minus one term in the base current.

$$I_B(V_{BE}, T, \beta) \approx \frac{I_0}{(\beta + 1)} e^{eV_{BE}/kT}$$

The effective AC signal resistance of base-emitter junction is

$$h_{ie} \equiv \left( \frac{\partial V_{BE}}{\partial I_B} \right)_{V_{CE}} = \left( \frac{\partial I_B}{\partial V_{BE}} \right)_{V_{CE}}^{-1} = \frac{(\beta + 1) kT}{e I_0} e^{-eV_{BE}/kT} = \frac{(\beta + 1) kT}{e I_0 e^{eV_{BE}/kT}} = \frac{kT}{e I_B} = \frac{\beta kT}{e I_C}$$
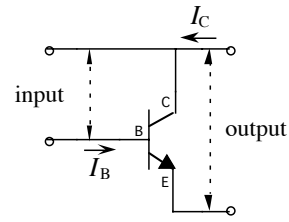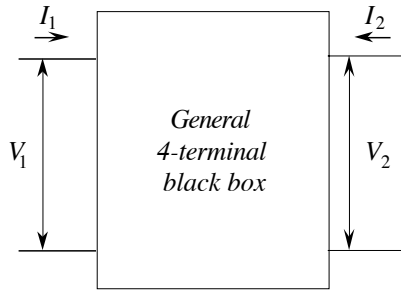
### Common Collector Configuration (Emitter Follower)



Common Collector

$$I_1 \rightarrow I_B, \quad V_1 \rightarrow V_{BE}, \quad I_2 \rightarrow I_C, \quad V_2 \rightarrow V_{CE}$$

Figure 7

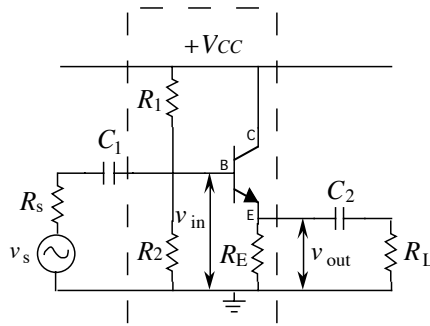


Figure 8

Application of Kirchhoff's and Ohm's Laws	
<p>(a) <math>v_1 = h_{11}i_1 + h_{12}v_2</math></p> <p>(b) <math>v_{in} = v_1 + v_{out}</math></p>	<p>(c) <math>i_2 = h_{21}i_1 + h_{22}v_2</math></p> <p>(d) <math>v_{out} = i_{R_E} R_E = i_{R_L} R_L = -v_2</math></p>
<p>(e) <math>i_1 + i_2 = i_E = i_{R_E} + i_{R_L}</math> (from current conservation)</p>	

Table 6

#### Current Gain

$$A_i = \frac{i_{out}}{i_1} = \frac{i_{R_L}}{i_1}$$

$$1) \quad i_1 + i_2 = i_{R_E} + i_{R_L}$$

$$2) \quad i_2 = h_{21}i_1 + h_{22}v_2$$

$$(1 + h_{21})i_1 + \left( h_{22} + \frac{1}{R_E} + \frac{1}{R_L} \right) v_2 = 0$$

$$3) \quad v_2 = i_{R_L} R_L$$

$$(1 + h_{21})i_1 + \left( h_{22} + \frac{1}{R_E} + \frac{1}{R_L} \right) (-i_{R_L} R_L) = 0$$

$$\begin{aligned} A_i &= \frac{(1 + h_{21})}{1 + \frac{R_L}{R_E} + h_{22}R_L} \\ &= \frac{(1 + h_{fe})}{1 + \frac{R_L}{R_E} + h_{oe}R_L} \approx h_{21} = h_{fe} \end{aligned}$$

### **Voltage Gain**

$$A_v = \frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_1 + v_{out}}$$

$$1) \quad i_1 + i_2 = i_{R_E} + i_{R_L}$$

$$2) \quad i_2 = h_{21}i_1 + h_{22}v_2$$

$$(1 + h_{21})i_1 + \left( h_{22} + \frac{1}{R_E} + \frac{1}{R_L} \right) v_2 = 0$$

$$i_1 = - \frac{\left( h_{22} + \frac{1}{R_E} + \frac{1}{R_L} \right)}{(1 + h_{21})} v_2$$

$$3) \quad v_1 = h_{11}i_1 + h_{12}v_2$$

$$v_1 = \left[ h_{12} - \frac{h_{11} \left( h_{22} + \frac{1}{R_E} + \frac{1}{R_L} \right)}{(1 + h_{21})} \right] v_2 = \left[ \frac{h_{11} \left( h_{22} + \frac{1}{R_E} + \frac{1}{R_L} \right)}{(1 + h_{21})} - h_{12} \right] v_{out}$$

$$\begin{aligned}
A_v &= \frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_1 + v_{out}} \\
&= \frac{v_{out}}{\left\{ \left[ \frac{h_{11} \left( h_{22} + \frac{1}{R_E} + \frac{1}{R_L} \right)}{(1 + h_{21})} - h_{12} \right] + 1 \right\} v_{out}} \\
&= \frac{1 + h_{21}}{(1 - h_{12})(1 + h_{21}) + h_{11}h_{22} + \frac{h_{11}}{R_E} + \frac{h_{11}}{R_L}} \\
&= \frac{1 + h_{fe}}{(1 - h_{re})(1 + h_{fe}) + h_{ie}h_{oe} + \frac{h_{ie}}{R_E} + \frac{h_{ie}}{R_L}} \approx 1
\end{aligned}$$

The voltage gain can be seen to be almost exactly 1.0. If the base-emitter junction is forward biased,  $V_{BE}$  will remain essentially constant at 0.6V for a silicon transistor. If the input changes by  $\Delta V$ ,  $V_B$  changes by  $\Delta V$  and  $V_E$  will change by approximately the same amount to keep  $V_{BE}$  constant. The output voltage change approximately equals the input voltage change  $\Delta V_E = (0.98 \text{ or } 0.99) \times \Delta V_B$ . The change in emitter voltage is in phase with the change in base voltage.

### **Input Impedance**

$$Z_{in} = \frac{v_{in}}{i_{in}}$$

The input impedance looking into the base of the transistor is

$$Z_{B_{in}} = h_{11} + (1 + h_{21})(R_E \parallel R_L) = h_{ie} + (1 + h_{fe})(R_E \parallel R_L)$$

The input impedance of the circuit is the parallel combination of the base resistors  $R_1$  and  $R_2$  and the input impedance looking into the base of the transistor.

$$Z_{in} = \frac{1}{\frac{1}{R_1 \parallel R_2} + \frac{1}{h_{ie} + [(1 + h_{fe})(R_E \parallel R_L)]}} \approx \frac{1}{\frac{1}{R_1 \parallel R_2} + \frac{1}{h_{ie} + h_{fe}(R_E \parallel R_L)}}$$

***Output Impedance***

The output impedance looking back into the emitter of the transistor is

$$\begin{aligned}
 Z_{out} &= \frac{v_{out}}{i_{out}} \\
 &= \frac{1}{\frac{1}{R_E} + h_{22} + \frac{1}{\frac{(R_1 \parallel R_2 \parallel R_S) + h_{11}}{(1 + h_{21})}}} \\
 &= \frac{1}{\frac{1}{R_E} + h_{oe} + \frac{1}{\frac{(R_1 \parallel R_2 \parallel R_S) + h_{ie}}{(1 + h_{fe})}}} \approx \frac{1}{\frac{1}{R_E} + \left[ \frac{(R_1 \parallel R_2 \parallel R_S) + h_{ie}}{h_{fe}} \right]}
 \end{aligned}$$